

# 1 Capacitors and DC Circuits

## 1.1 Formulas

Definition of capacitance:  $C = Q/V$

Energy stored in a capacitor:

$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2 = \frac{1}{2}QV$$

Parallel plate capacitance w/o dielectric:  $C = \epsilon_0 A/d$

Parallel plate capacitance w/ dielectric:  $C = \kappa\epsilon_0 A/d$

Capacitors in series:  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$

Capacitors in parallel:  $C = C_1 + C_2 + \dots + C_n$

Definition of current:  $i = \Delta Q/\Delta t$

Current and drift velocity:  $I = nqv_d A$

Definition of resistance:  $R = \Delta V/I$

Resistance of a wire:  $R = \rho l/A$

Temperature variation of resistivity:

$$\rho = \rho_0[1 + \alpha(T - T_0)]$$

Power dissipation in a resistor:

$$P = I\Delta V = I^2 R = \frac{\Delta V^2}{R}$$

Steps: in application of Kirchhoff's Rules

- Label current:  $i_1, i_2, i_3, \dots$
- Node equation:  $\sum i_{\text{in}} = \sum i_{\text{out}}$
- Loop equation:  $\sum (\pm V) + \sum \mp iR = 0$

Resistors in series:  $R = R_1 + R_2 + \dots + R_n$

Resistors in parallel:  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

Charging in an RC circuit:  $q(t) = Q(1 - e^{-t/RC})$


Discharging in an RC circuit:  $q(t) = Qe^{-t/RC}$ , where  $RC = \tau$  is the time constant.

## 1.2 Electrons Through a Resistor Problem

If  $5 \times 10^{21}$  electrons pass through a  $20\Omega$  resistor in 10 min, what is the potential difference across the resistor?  
The fundamental charge is  $1.602 \times 10^{-19}$  C. Answer in units of V.

## 1.3 Voltage across a capacitor problem


Consider the capacitor network

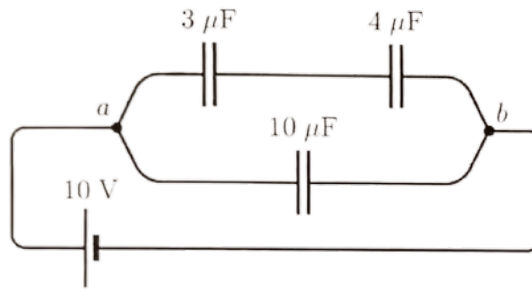

What is the voltage across the  $4\ \mu\text{F}$  (upper right hand) capacitor? Answer in units of V.
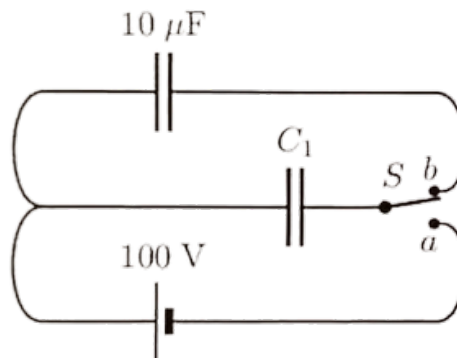
## 1.4 Unknown Capacitance Problem

When the switch is in position a, an isolated capacitor of unknown capacitance has been charged to a potential difference of 100 V. When the switch is moved to position b, this charged capacitor is then connected parallel to the uncharged  $10\ \mu\text{F}$  capacitor. The voltage across the combination becomes 30 V.



Calculate the unknown capacitance. Answer in units of  $\mu\text{F}$ .


## 1.5 Drift Velocity Problem

An aluminum wire with a cross-sectional area of  $4 \times 10^{-6}\ \text{m}^2$  carries a current of 5 A.

Find the drift speed of the electrons in the wire. Assume that each atom supplies one electron. Aluminum has a molecular weight of 26.98 g/mol and a density of  $2.7\ \text{g/cm}^3$ . Avogadro's number is  $6.022 \times 10^{23}$  and the fundamental charge is  $1.602 \times 10^{-19}\ \text{C}$ . Answer in units of m/s.
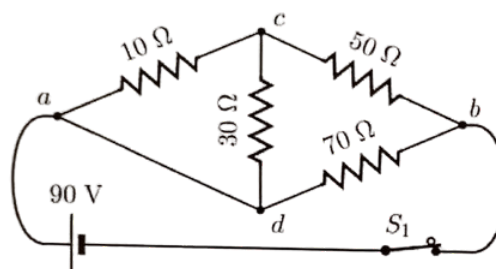
## 1.6 Equivalent Resistance Problem


Four resistors are connected as shown in the figure.



Find the resistance between points a and b. Answer in units of  $\Omega$ .
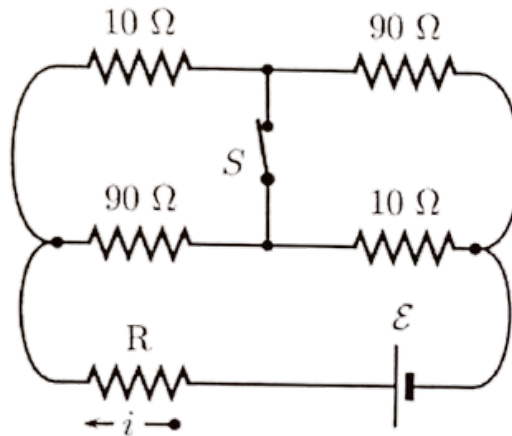
### 1.7 Find $R$ in Circuit with Switch Problem


In the circuit shown below, the current  $i$  in the resistor  $R$  doubles its original value when the switch  $S$  is closed.



Find the value of  $R$ . Answer in units of  $\Omega$ .
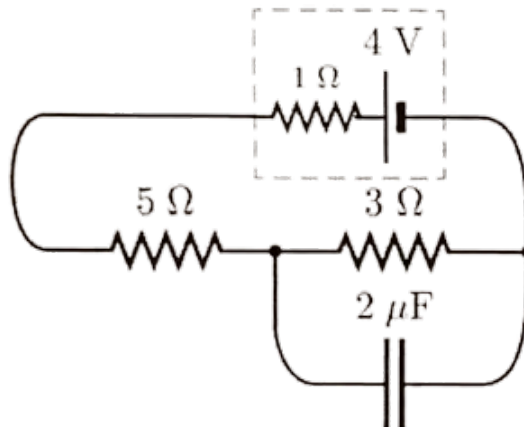
### 1.8 Charge on Capacitor Problem


In the figure below the battery has an emf of 4 V and an internal resistance of  $1\Omega$ . Assume there is a steady current flowing in the circuit.



Find the charge on the  $2\mu\text{F}$  capacitor. Answer in units of  $\mu\text{C}$ .
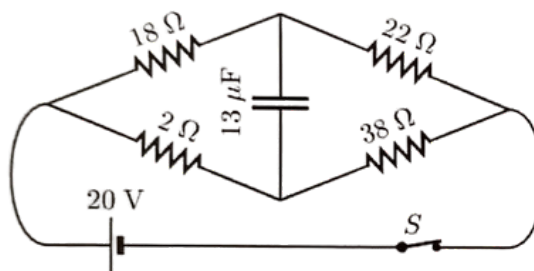
### 1.9 Voltage across Capacitor Problem


The circuit has been connected as shown in the figure for a “long” time.



What is the magnitude of the electric potential across the capacitor? Answer in units of V.

## 1.10 Two Loop Circuit Problem

Consider the circuit

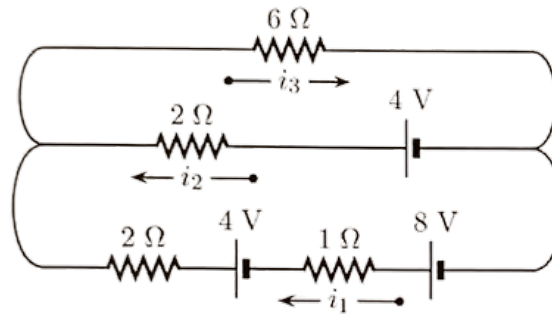

Find  $i_1$ . Answer in units of A.